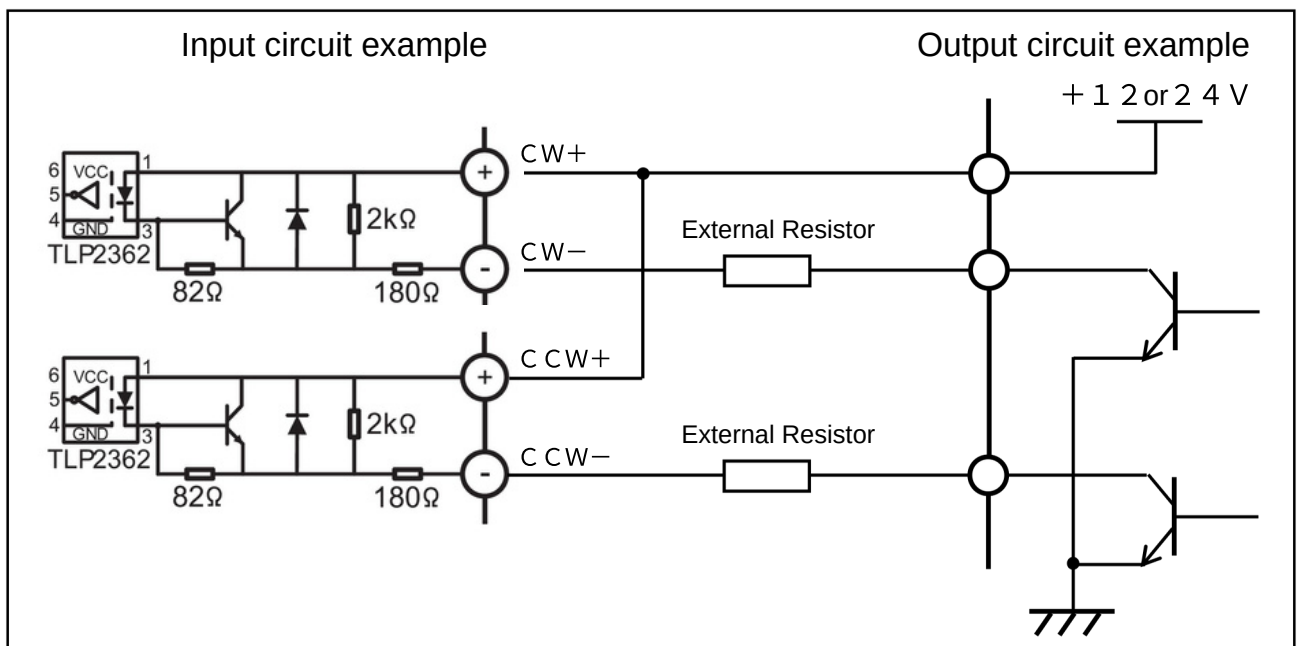


Our drivers support 5V signal input as standard. When 12V or 24V signals are input over the range described in the manual, an external resistor must be added as shown in the diagram below.



The external resistance is calculated as follows:

- Input forward current of the photocoupler: I_F
- Input forward voltage of photocoupler: V_F

$$(\text{Internal resistance} + \text{External resistance}) \times I_F + V_F = \text{Input voltage}$$

↓

$$\text{External resistance} = (\text{Input voltage} - V_F) / I_F - \text{Internal resistance}$$

Substituting the following values into this formula

- Forward current $I_F = 12\text{mA}$
- Photocoupler input forward voltage $V_F = 1.5\text{V}$
- Internal resistance $82 + 180 = 262\Omega$ (for the resistance value shown in the diagram)

The external resistance value is as follows.

- Input voltage = 12V External resistance = $613\Omega \rightarrow 620\Omega$ recommended
- Input voltage = 24V External resistance = $1613\Omega \rightarrow 1.6\text{K}\Omega$ recommended

Note: Depending on the model and production date, there may be products with an internal resistance value of 270Ω or 390Ω . In this case, calculate as above or refer to the table below.

External Resistance Table

		Input voltage	
		12 V	24 V
Internal Resistance	262Ω	613Ω (620 Ω recommend)	1613Ω (1.6K Ω recommend)
	270Ω	605Ω (620 Ω recommend)	1605Ω (1.6K Ω recommend)
	390Ω	485Ω (470 Ω recommend)	1485Ω (1.5K Ω recommend)

To prevent burnout, use 1/2W type external resistors.